



NATIONAL OPEN UNIVERSITY OF NIGERIA
PLOT 91, CADASTRAL ZONE, NNAMDI AZIKIWE EXPRESSWAY, JABI - ABUJA
FACULTY OF SCIENCES
DEPARTMENT OF PHYSICS
2025_2 EXAMINATIONS

COURSE CODE: PHY310
COURSE TITLE: ELECTRONICS I
CREDIT UNIT: 2
TIME ALLOWED: (2 HRS)
INSTRUCTION: *Answer question 1 and any other three questions*

Question 1

- i. Define the following terms: Depletion, Enhancement, P-Channel, N – Channel and Ohmic mode 10 marks
- ii. What are passive filters 5marks
- iii. Draw the circuit diagram for the Passive Wien bridge filter 5marks
- iv. Sketch a 4-element low-pass active filter 5marks

Question 2

- i. What are amplifiers? 4marks
- ii. Sketch the cross-sectional of an n-type MOSFET transistor and explain the functions of each. 6marks
- iii. Discuss briefly the operations of the JFET Transistor 5marks

Question 3

- i. What are high-frequency power amplifiers?
- ii. List 5 main characteristics of an amplifier
- iii. Sketch and describe briefly the operations of Class A and AB amplifiers

Question 4

- i. Define the following terms i. electric current ii. Electric potential iii. Electric charge iv. Electrical energy
- ii. Discuss briefly the following i. Half wave rectifier ii. Full rectifier
- iii. With the aid of a perfect circuit diagram describe the following i. shunt regulator ii. Series regulator iii. Darlington buffered regulator

Question 5

- i. What are filters
- ii. Discuss briefly passive and active filters
- iii. Discuss briefly the Hum injector filter